

# EG25-G

# Reference Design

**LTE Module Series**

Rev. EG25-G\_Reference\_Design\_V1.0

Date: 2018-12-18

Status: Released



**Our aim is to provide customers with timely and comprehensive service. For any assistance, please contact our company headquarters:**

**Quectel Wireless Solutions Co., Ltd.**

7<sup>th</sup> Floor, Hongye Building, No.1801 Hongmei Road, Xuhui District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: [info@quectel.com](mailto:info@quectel.com)

**Or our local office. For more information, please visit:**

<http://www.quectel.com/support/sales.htm>

**For technical support, or to report documentation errors, please visit:**

<http://www.quectel.com/support/technical.htm>

Or email to: [support@quectel.com](mailto:support@quectel.com)

**GENERAL NOTES**

QUECTEL OFFERS THE INFORMATION AS A SERVICE TO ITS CUSTOMERS. THE INFORMATION PROVIDED IS BASED UPON CUSTOMERS' REQUIREMENTS. QUECTEL MAKES EVERY EFFORT TO ENSURE THE QUALITY OF THE INFORMATION IT MAKES AVAILABLE. QUECTEL DOES NOT MAKE ANY WARRANTY AS TO THE INFORMATION CONTAINED HEREIN, AND DOES NOT ACCEPT ANY LIABILITY FOR ANY INJURY, LOSS OR DAMAGE OF ANY KIND INCURRED BY USE OF OR RELIANCE UPON THE INFORMATION. ALL INFORMATION SUPPLIED HEREIN IS SUBJECT TO CHANGE WITHOUT PRIOR NOTICE.

**COPYRIGHT**

THE INFORMATION CONTAINED HERE IS PROPRIETARY TECHNICAL INFORMATION OF QUECTEL WIRELESS SOLUTIONS CO., LTD. TRANSMITTING, REPRODUCTION, DISSEMINATION AND EDITING OF THIS DOCUMENT AS WELL AS UTILIZATION OF THE CONTENT ARE FORBIDDEN WITHOUT PERMISSION. OFFENDERS WILL BE HELD LIABLE FOR PAYMENT OF DAMAGES. ALL RIGHTS ARE RESERVED IN THE EVENT OF A PATENT GRANT OR REGISTRATION OF A UTILITY MODEL OR DESIGN.

***Copyright © Quectel Wireless Solutions Co., Ltd. 2018. All rights reserved.***

# About the Document

## History

Revision	Date	Author	Description
1.0	2018-12-18	Lorry XU	Initial

---

## Contents

About the Document .....	2
Contents .....	3
<b>1 Reference Design</b> .....	<b>4</b>
1.1. Introduction .....	4
1.2. Schematics .....	4

# 1 Reference Design

## 1.1. Introduction








This document provides the reference design for Quectel EG25-G module.

## 1.2. Schematics

The schematics illustrated in the following pages are provided for your reference only.



# MCU Interface

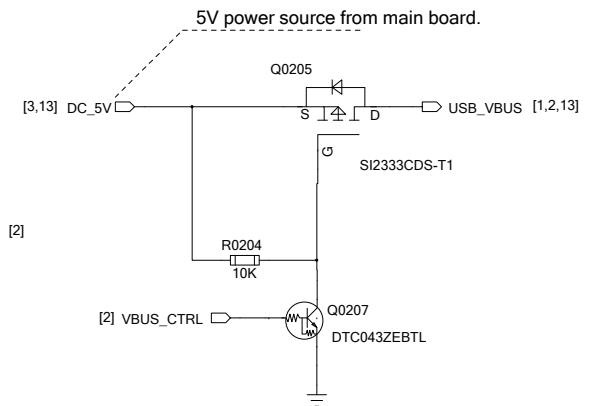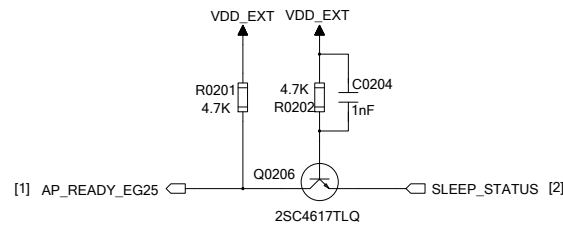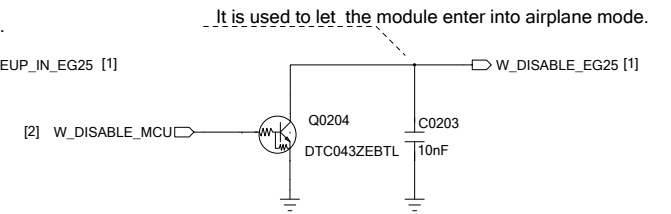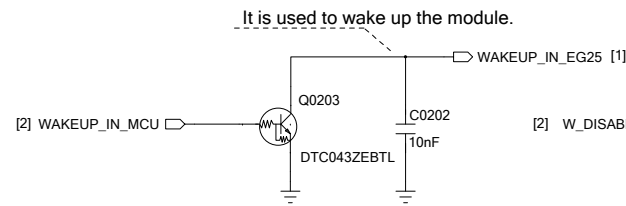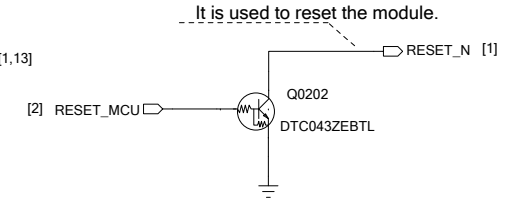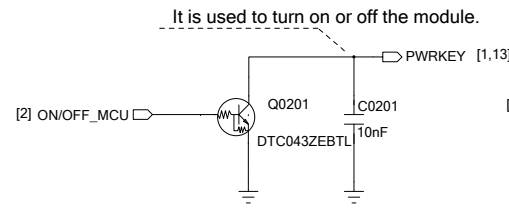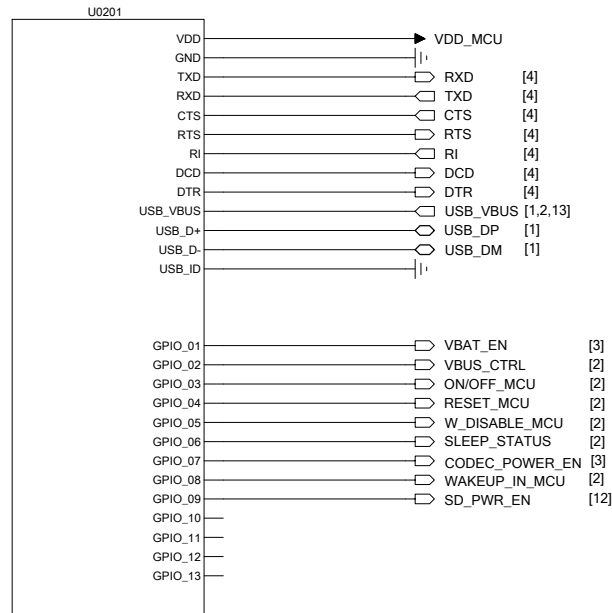

## Notes:


- U0201 represents customers's MCU. The power domain of GPIO interfaces on EG25-G modules is 1.8V. If the domain on U0201's GPIO interfaces is the same, then the level translation circuit can be omitted.
- EG25 can only work as a USB device and supports Full Speed and High Speed modes. To communicate with USB interface, MCU needs to support USB host or OTG function. The USB\_VBUS pins of MCU and EG25 should be powered by a 5V power system for USB detection, and VBUS\_CTRL is used to turn on/off USB\_VBUS power supply.
- AP\_READY is used to detect the MCU's sleep state. For more details, please refer to *Quectel\_EG25-G\_Hardware\_Design*.
- WAKEUP\_IN\_EG25 should be kept at low level before the module starts up successfully.

Quectel Wireless Solutions		
DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET	2 OF 13	DATE 2018/12/18


# Power Supply Design
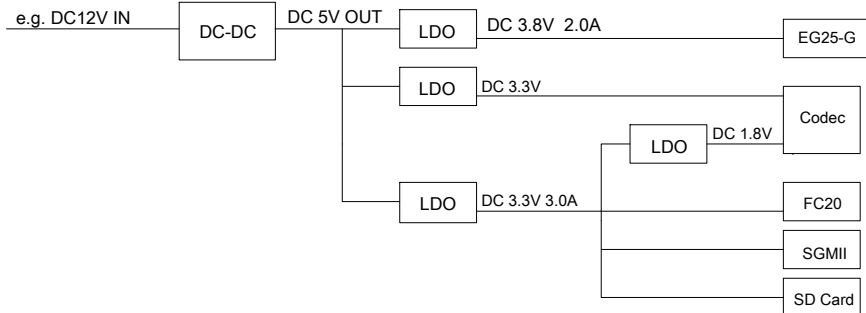
## DC-DC Application

It is used when the input voltage is above 7V. Use DC-DC converter to convert a high input voltage into a 5V output, and then the LDOs will generate 3.8V, 3.3V and 1.8V typical voltages.



## VBAT Design

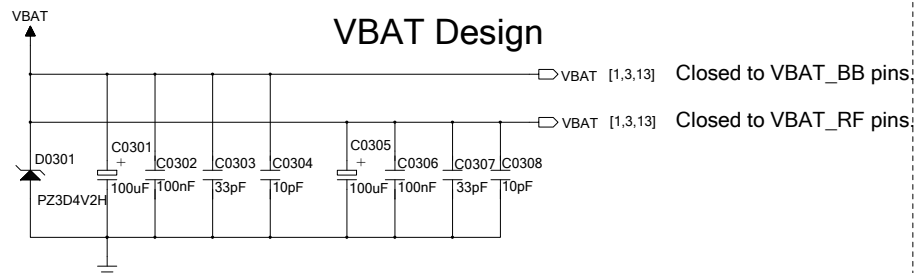


Notes:


1. The power supply must be able to provide sufficient current up to 2A or more.
2. VBAT should be routed in star mode to VBAT\_BB and VBAT\_RF pins.
3. The recommended operating voltage of VBAT is 3.3V~4.3V.
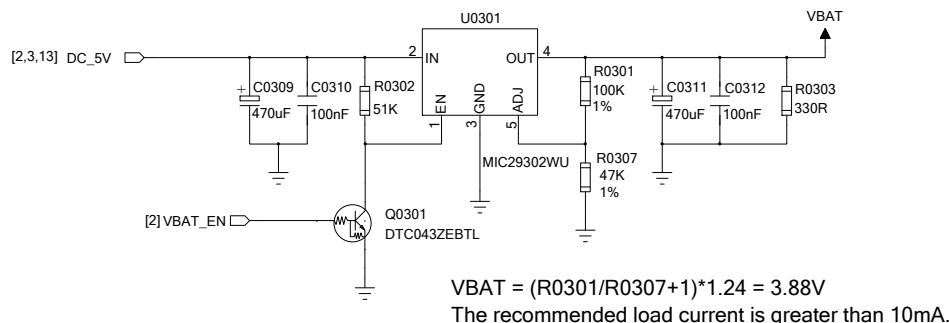
## LDO Application

It is used when the input voltage is below 7V.




## Power Supply for PCM Codec

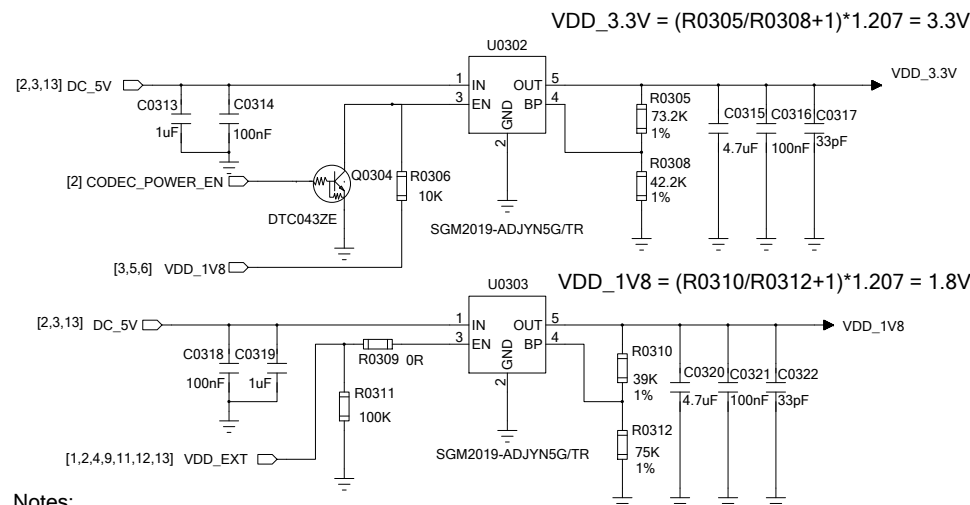

Notes:

1. CODEC\_POWER\_EN must be at low level in order to ensure the normal output voltage of VDD\_3.3V. If VDD\_3.3V power supply needs to be switched off, please keep CODEC\_POWER\_EN at high level.
2. The following power-on/off sequences should be complied with to ensure the audio codec works normally.  
Power-on Sequence: power on VDD\_1V8 first, then VDD\_3.3V.  
Power-off Sequence: power off VDD\_3.3V first, then VDD\_1V8.
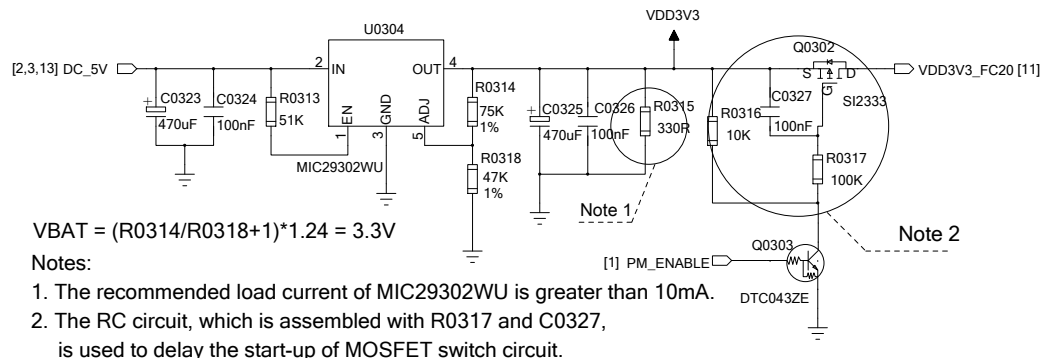
## Power Supply for FC20, SGMII and SD Card




### Quectel Wireless Solutions

DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET 3 OF 13	DATE 2018/12/18	



# (U)SIM and UART Designs


## (U)SIM Interface

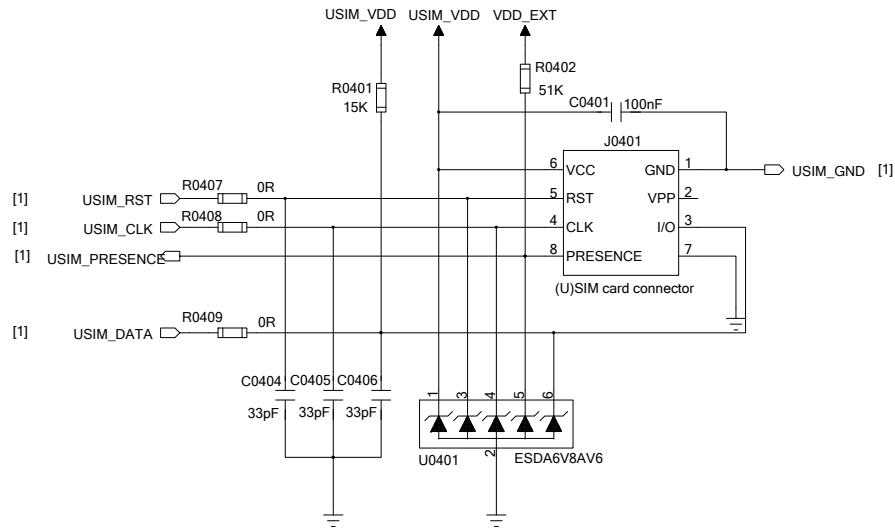


### Notes:

- U401 is recommended to be used to offer good ESD protection, and the parasitic capacitance should not be more than 15pF.
- It is recommended to connect the (U)SIM card connector's GND to the module's USIM\_GND. If the ground is complete on customers' PCB, USIM\_GND can be connected to PCB ground directly.
- The pull-up resistor R0401 can improve anti-jamming capability, and should be placed close to the (U)SIM card connector.
- R0407~R0409 are used for debugging, C0404~C0406 are used for filtering interference of GSM900MHz.
- C0401 capacitance should be less than 1uF, and should be placed close to the (U)SIM card connector.
- For more information about the layout, please refer to *Quectel\_EG25-G\_Hardware\_Design*.
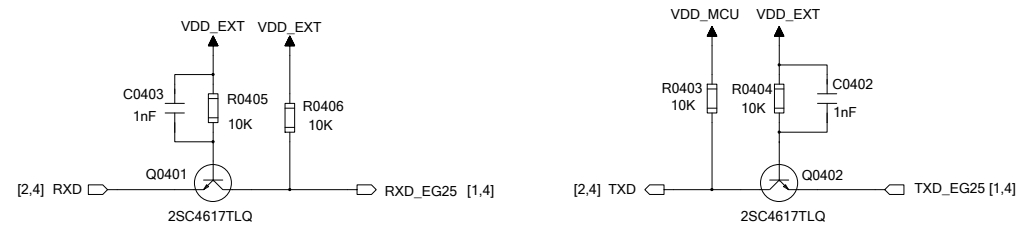
## UART Translation - Transistor Solution



## UART Translation - IC Solution

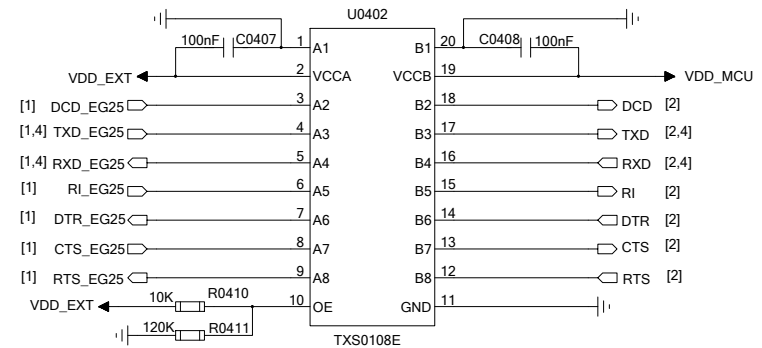


### Notes:

- There are two translation solutions: transistor solution and IC solution, and it is recommended to select the IC solution.
- The power supply voltage of VCCA should not exceed that of VCCB. For more information about TXS0108E, please refer to the datasheet from TI.
- The transistor circuit solution is not suitable for applications with high baud rates exceeding 460Kbps. The 1nF capacitors C0402 and C0403 can improve the signal quality.
- The RTS and DTR transistor circuits are similar to that of RXD interface. The CTS, RI and DCD transistor circuits are similar to that of TXD interface.

### Quectel Wireless Solutions

DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET 4 OF 13	DATE 2018/12/18	

# Audio Codec Design (ALC5616)

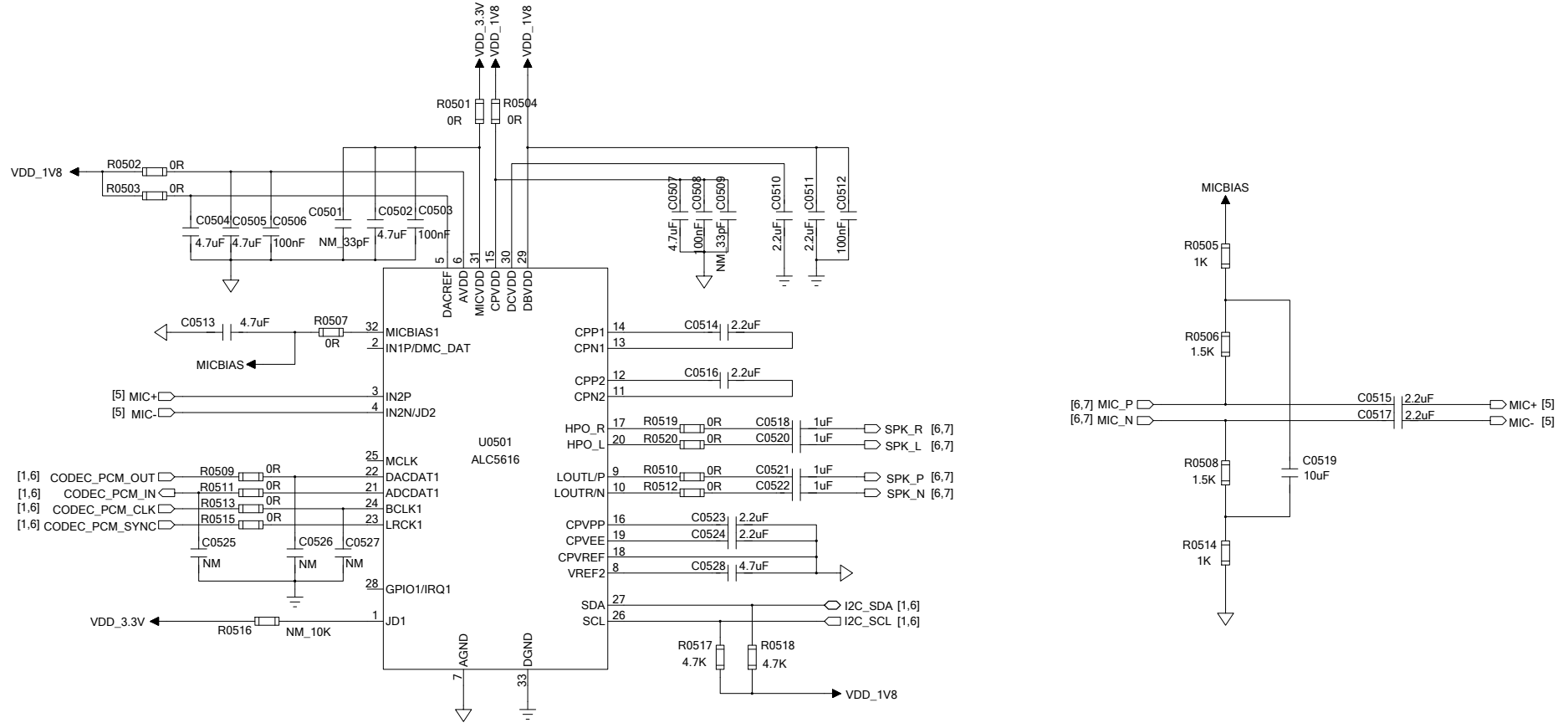


**Notes:**

1. ALC5616 power-on sequence: DBVDD/I2C pull-up power/AVDD/DACREF/CPVDD -> MICVDD -> software initialization.
2. ALC5616 power-off sequence: close codec function by software -> MICVDD -> DBVDD/I2C pull-up power/AVDD/DACREF/CPVDD.
3. EG25-G module will automatically initialize the codec via I2C interface after it is turned on successfully, so all power supplies for the codec need to be powered on before that.
4. Pin AGND and DGND of ALC5616 are connected together through 0R resistor R0703 in Sheet 7.

Quectel Wireless Solutions		
DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET	5 OF 13	DATE 2018/12/18

# Audio Codec Design (TLV320AIC3104)

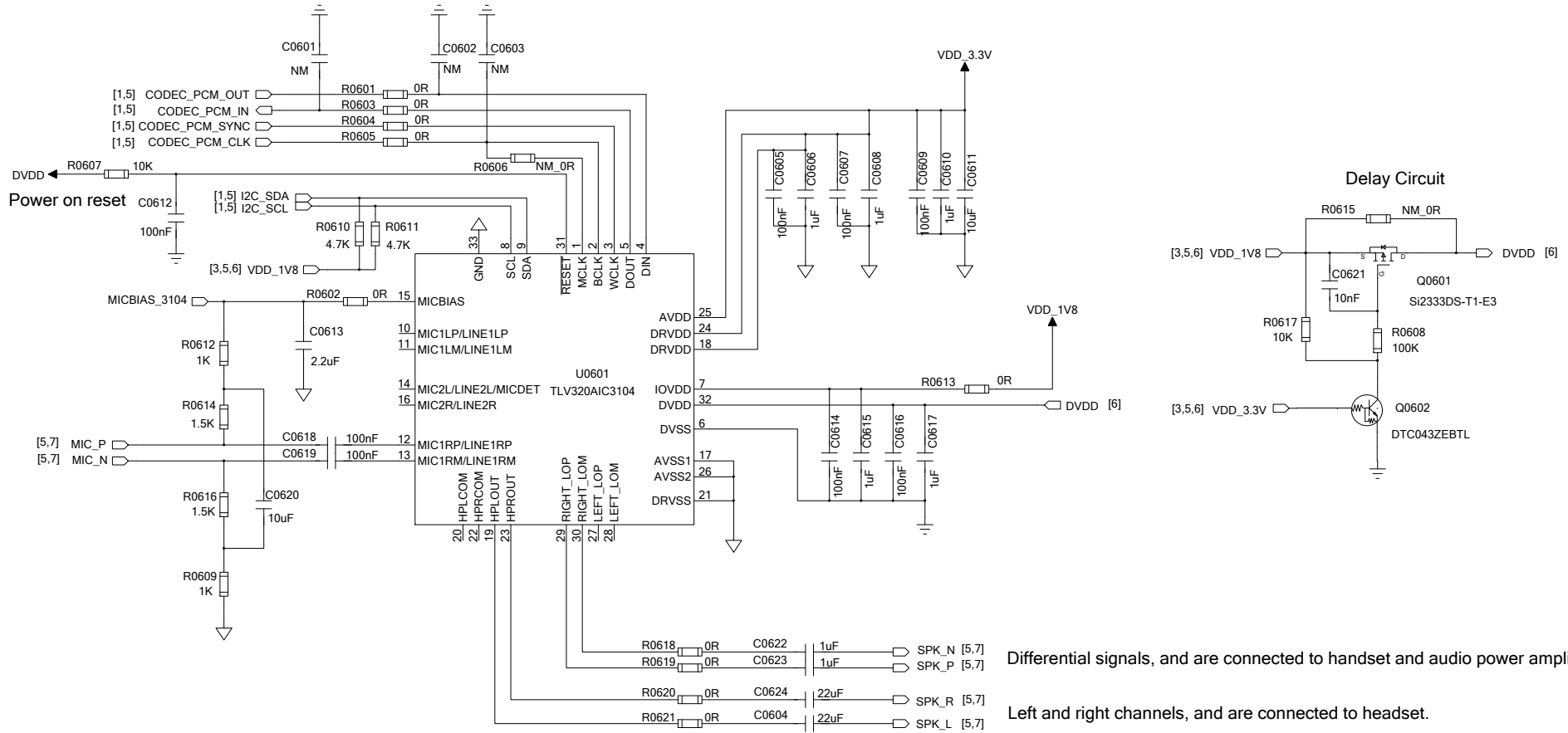

Differential signals, and are connected to handset and audio power amplifier.

Left and right channels, and are connected to headset.


**Notes:**

1. TLV320AIC3104 power-on sequence: IOVDD -> AVDD/DRVDD -> DVDD -> software initialization.
2. The RC delay circuit, which is assembled with C0621 and R0608, is used to ensure that the power-on time difference between AVDD and DVDD is within 5ms.
3. The RESET pin must be driven at low level for at least 10ns after all power supplies for TLV320AIC3104 are at their specified values.
4. EG25-G module will automatically initialize the codec via I2C interface after it is turned on successfully, so all power supplies for the codec need to be powered on before that.
5. The AGND and DGND of TLV320AIC3104 are connected together through 0R resistor R0703 in Sheet 7.


Quectel Wireless Solutions		
DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET 6 OF 13	DATE 2018/12/18	

# Audio Interfaces

## Handset Application

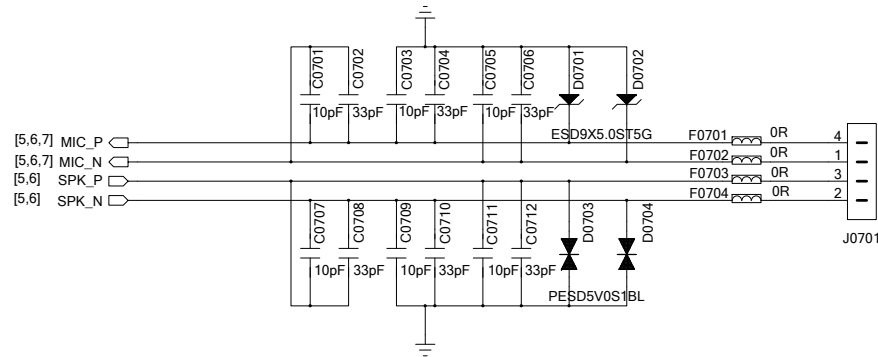

## Earphone Application

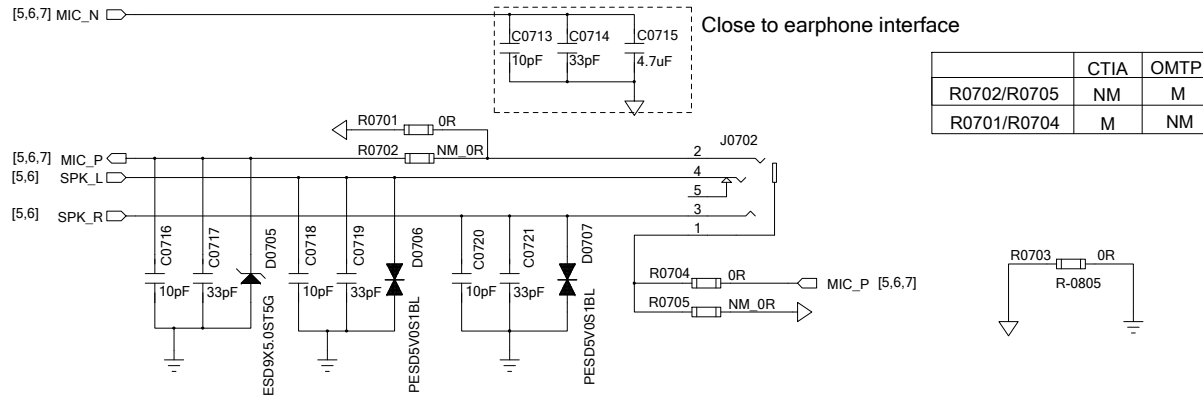

	CTIA	OMTP
R0702/R0705	NM	M
R0701/R0704	M	NM

**Notes:**


1. The analog output only drives earphone and headset. For larger power loads such as speakers, an audio power amplifier should be added in the design.
2. In handset application, both the MIC and SPK signal traces need to be routed as differential pairs.
3. In earphone application, the MIC signal traces need to be routed as differential pairs.
4. All MIC and SPK signal traces should be routed with total grounding and far away from noise such as clock and DC-DC signals, etc.
5. ALC5616 and TLV320AIC3104 cannot be used simultaneously in audio codec design.

### Quectel Wireless Solutions


DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET	7 OF 13	DATE 2018/12/18

# RF and GNSS Designs


## Main Antenna Circuit

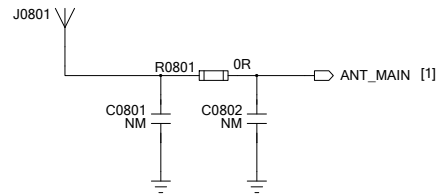


## Diversity Antenna Circuit

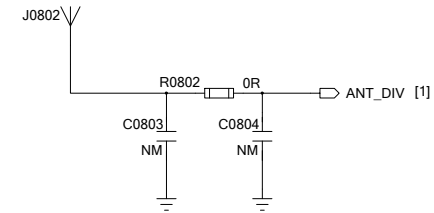

## GNSS Antenna Circuit

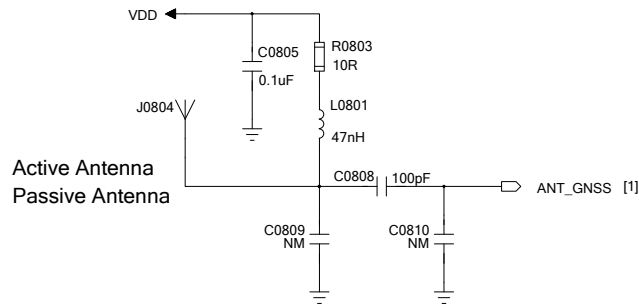

## FC20 Antenna Circuit

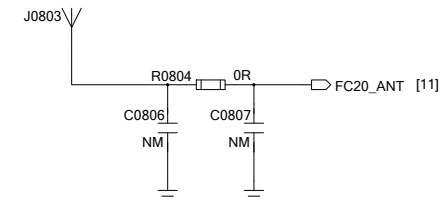


### Notes:

1. It is recommended to use PI type main/Rx-diversity/FC20 antenna circuit, thus ensuring convenient subsequent debugging.
2. The diversity reception function is ON by default. If diversity antenna is not used, there is a need to use AT command to turn off diversity reception.
3. An external LDO can be selected to supply power for active antenna.
4. If passive antenna is used, then R0803 and L0801 are not needed.
5. The impedance of the RF signal traces must be controlled as 50Ω when routing.

### Quectel Wireless Solutions

DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET	8 OF 13	DATE 2018/12/18

# Ethernet PHY Design


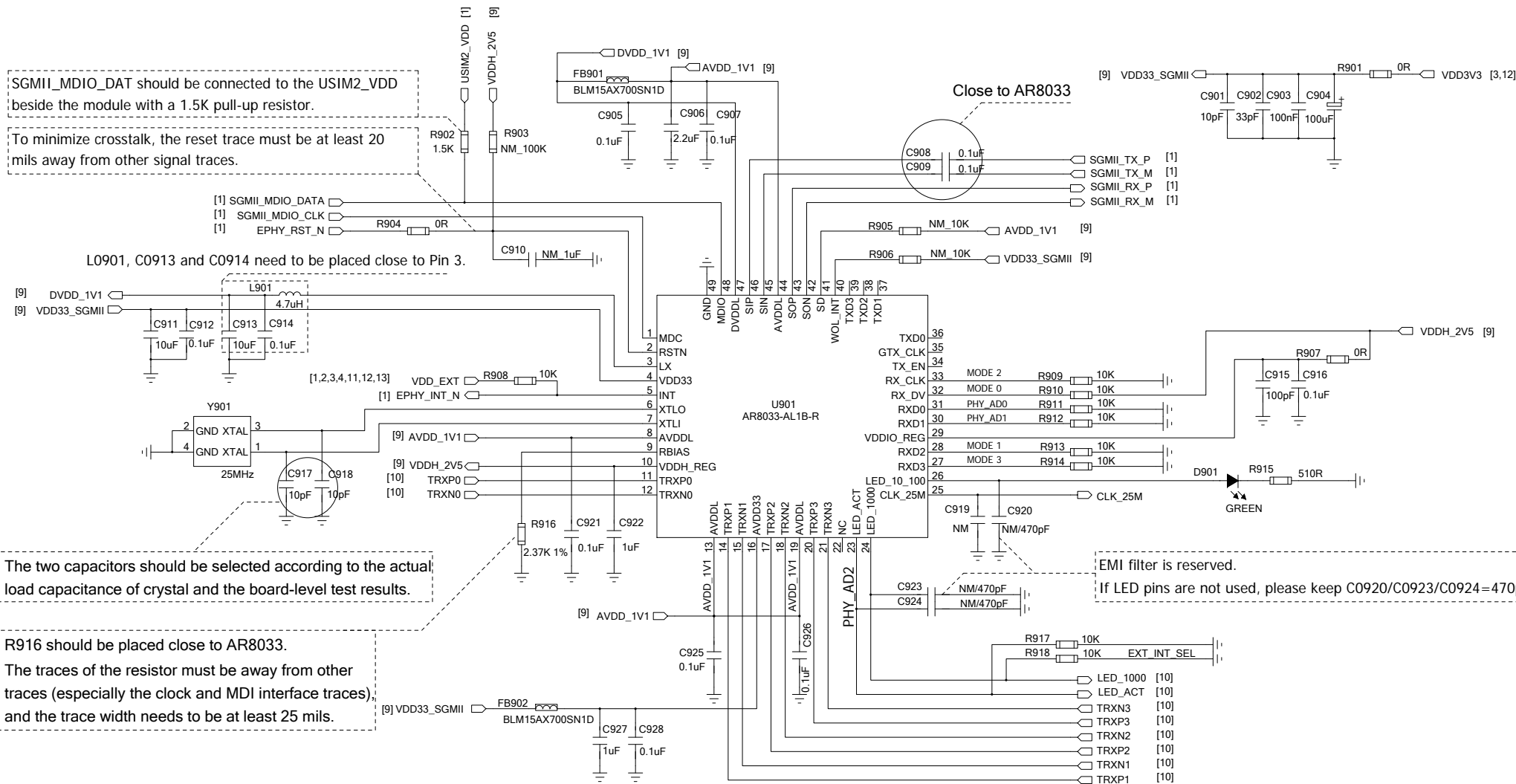


**Notes:**

- In the following description, the SGMII data signal refers to the SGMII TX and RX difference pair, and the SGMII control signal refers to the SGMII\_MDIO\_CLK, SGMII\_MDIO\_DATA, EPHY\_RST\_N and EPHY\_INT\_N.
- SGMII data and control signals should be strictly protected with ground and kept away from RF, analog, clock and DCDC signals etc.
- Keep the maximum trace length of SGMII data signal less than 10-inch and keep skew of the TX and RX signals less than 20mil.
- The differential impedance of SGMII data signal is  $100\Omega \pm 10\%$ , and the reference ground of the area should be complete.
- Make sure the trace spacing between SGMII RX and TX is at least 3 times of the trace width, and is the same to the adjacent signal traces.
- The peripheral circuit layout of Ethernet PHY chip AR8033 should be designed on a four-layer PCB, and the second layer should be total grounded as the AR8033 reference GND.
- RJ45, network transformer, AR8033, and the SGMII interface should be placed as close as possible.

Quectel Wireless Solutions		
DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET 9 OF 13	DATE 2018/12/18	

# Ethernet Network Port Design

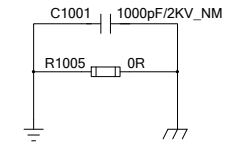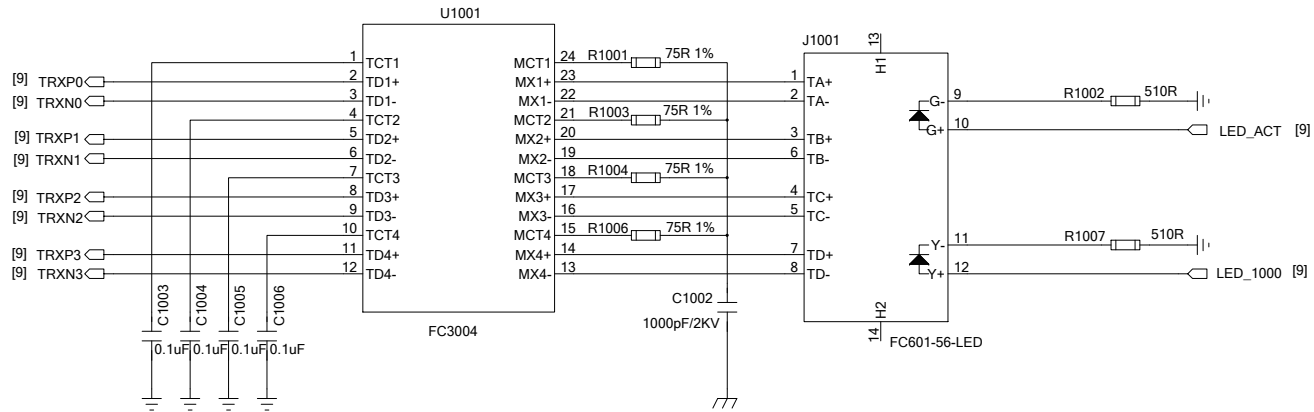

PHY core configuration signal	Description	Default internal weak pull-up/down	Application external weak pull-up/down
PHY_AD2	PHY_AD[2:0] set the lower three bits of the physical address. The upper two bits of the physical address are set to 00.	1	0
PHY_AD1		0	0
PHY_AD0		0	0
MODE 3	Mode select bit 3	0	0
MODE 2	Mode select bit 2	0	0
MODE 1	Mode select bit 1	0	0
MODE 0	Mode select bit 0	0	1
EXT_INT_SEL	An external 10K pull-down resistor is required.	1	0

0 = Pull-down, 1 = Pull-up.

## Notes:


1. Route MDI differential signals with  $100\Omega \pm 10\%$ , and the reference ground of the area should be complete.
2. Keep skew of the MDI differential signals less than 20mils, and the maximum trace length must be less than 10 inches.
3. To minimize crosstalk, the distance between separate adjacent pairs that are on the same layer must be equal to or larger than 40 mils.

Quectel Wireless Solutions		
DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET	10 OF 13	DATE 2018/12/18





# SD Card Interface Design

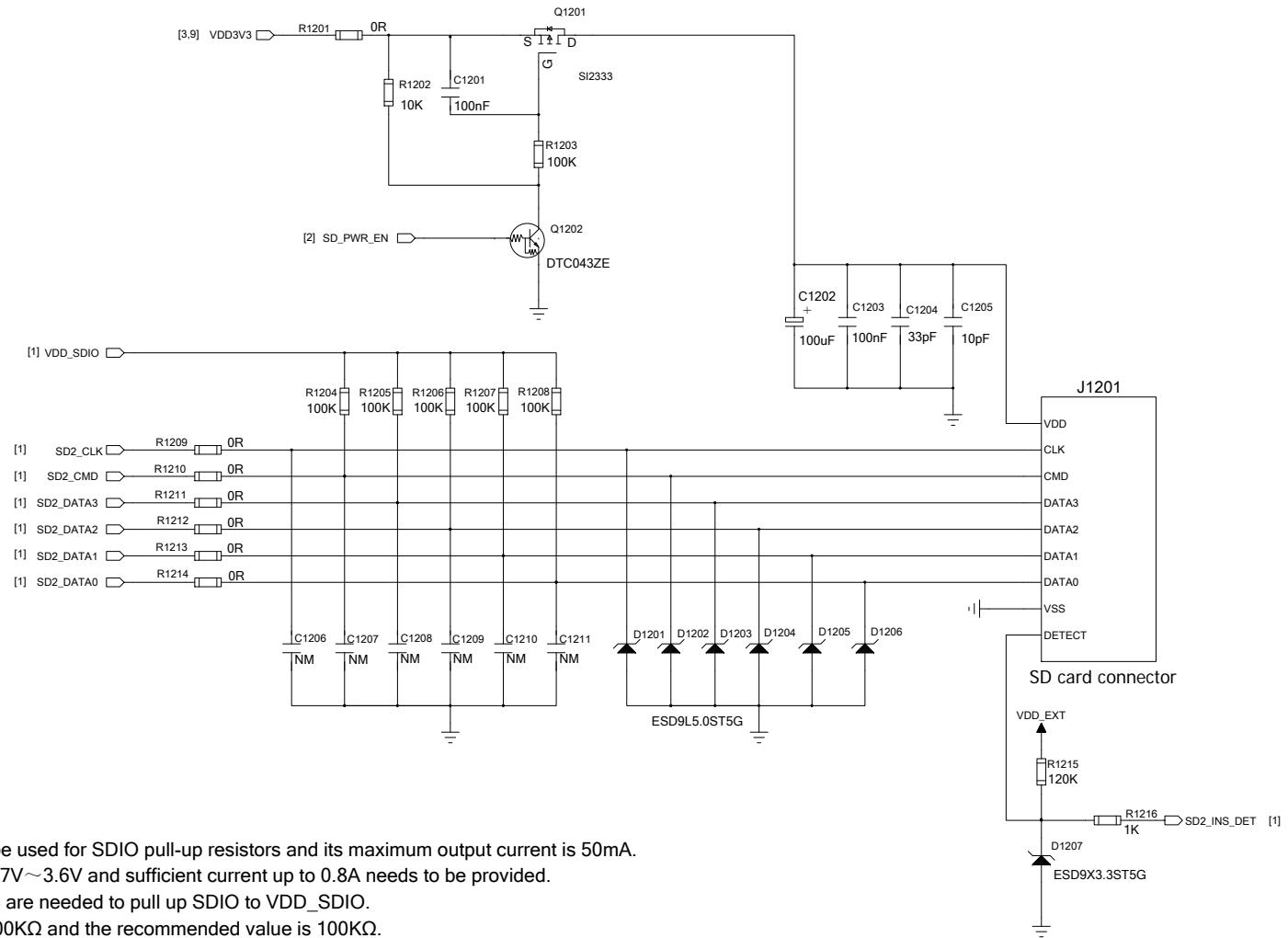

## Notes:


1. The pin 34 (VDD\_SDIO) on the module can only be used for SDIO pull-up resistors and its maximum output current is 50mA.
2. The supply voltage range of VDD for SD card is 2.7V~3.6V and sufficient current up to 0.8A needs to be provided.
3. To avoid the jitter of bus, resistors R1204~R1208 are needed to pull up SDIO to VDD\_SDIO.  
The value of these resistors is between 10KΩ~100KΩ and the recommended value is 100KΩ.
4. In order to adjust signal quality, it is recommended to add 0Ω resistors R1209~R1214 in series between the module and the SD card connector.  
The bypass capacitors C1206~C1211 are reserved and not mounted by default.
5. It is recommended to add ESD protection devices near the pins of SD card connector. The parasitic capacitance of ESD protection devices should be smaller than 15pF.
6. Keep SDIO signals far away from other sensitive circuits/signals such as RF circuits, analog signals, etc, as well as noisy signals such as clock and DC-DC signals, etc.
7. Route SDIO signals with 50Ω±10% impedance. It is important to route SDIO signals with total grounding, and the total trace length should be less than 23mm.
8. It is recommended to keep the trace length difference between CLK and DATA/CMD less than 1mm.
9. Make sure the adjacent trace spacing is two times of the trace width and the bus capacitance is less than 15pF.

## Quectel Wireless Solutions

DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET	12 OF 13	DATE 2018/12/18

# Other Designs


## Indicators

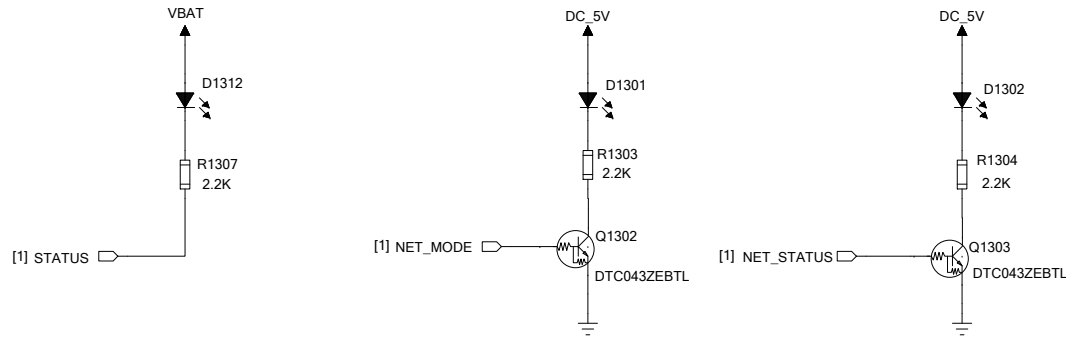

### Notes:


1. The STATUS is an open drain output pin, and its drive current is less than 1mA.
2. For more details about NET\_MODE and NET\_STATUS, please refer to *Quectel\_EG25-G\_Hardware\_Design*.
3. If the current consumption is required as low as possible when the device is in sleep, replace the power supply of indicators with controllable one. Turn off the power when the module enters into sleep mode.

## Reserved Test Points

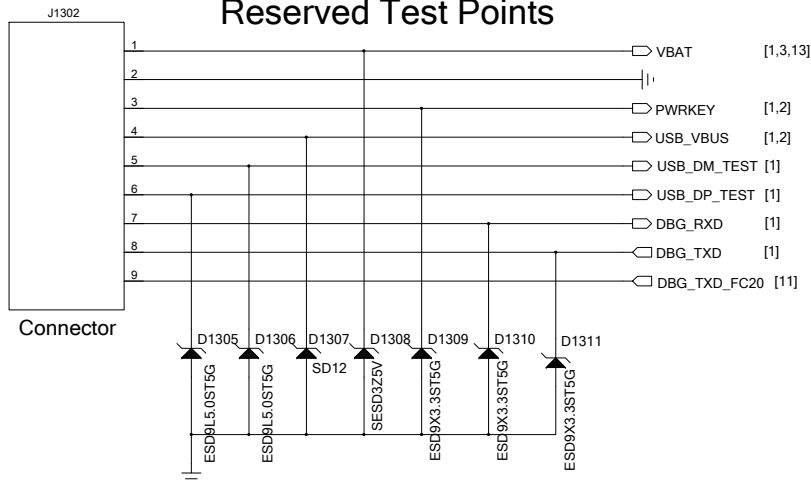

### Notes:

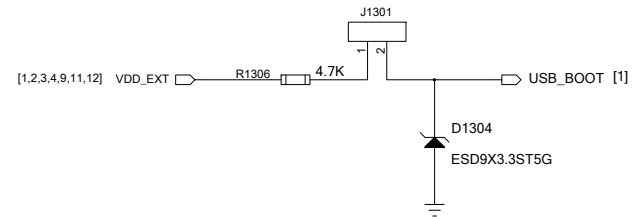1. Both USB and debug UART interfaces are reserved for software debugging.
2. USB interface also can be used to upgrade firmware.
3. Junction capacitance of ESD protection devices on USB data lines should be less than 1pF.
4. The module's debug UART interface supports 1.8V power domain, A level translator should be used if the power domain of customers' application is 3.3V.



### Notes:

1. It is recommended to reserve USB\_BOOT design.
2. USB\_BOOT is kept open by default. When it is at high level, the module will enter download mode.

## Quectel Wireless Solutions

DRAWN BY Lorry XU	PROJECT EG25-G	TITLE Reference Design
CHECKED BY Woody WU	SIZE A2	VER 1.0
SHEET 13 OF 13	DATE 2018/12/18	