

EC200A Series

Reference Design

LTE Standard Module Series

Version: 1.0.0

Date: 2021-08-31

Status: Preliminary



At Quectel, our aim is to provide timely and comprehensive services to our customers. If you require any assistance, please contact our headquarters:

Quectel Wireless Solutions Co., Ltd.

Building 5, Shanghai Business Park Phase III (Area B), No.1016 Tianlin Road, Minhang District, Shanghai 200233, China

Tel: +86 21 5108 6236

Email: info@quectel.com

Or our local offices. For more information, please visit:

<http://www.quectel.com/support/sales.htm>.

For technical support, or to report documentation errors, please visit:

<http://www.quectel.com/support/technical.htm>.

Or email us at: support@quectel.com.

Legal Notices

We offer information as a service to you. The provided information is based on your requirements and we make every effort to ensure its quality. You agree that you are responsible for using independent analysis and evaluation in designing intended products, and we provide reference designs for illustrative purposes only. Before using any hardware, software or service guided by this document, please read this notice carefully. Even though we employ commercially reasonable efforts to provide the best possible experience, you hereby acknowledge and agree that this document and related services hereunder are provided to you on an “as available” basis. We may revise or restate this document from time to time at our sole discretion without any prior notice to you.

Use and Disclosure Restrictions

License Agreements

Documents and information provided by us shall be kept confidential, unless specific permission is granted. They shall not be accessed or used for any purpose except as expressly provided herein.

Copyright

Our and third-party products hereunder may contain copyrighted material. Such copyrighted material shall not be copied, reproduced, distributed, merged, published, translated, or modified without prior written consent. We and the third party have exclusive rights over copyrighted material. No license shall be granted or conveyed under any patents, copyrights, trademarks, or service mark rights. To avoid ambiguities, purchasing in any form cannot be deemed as granting a license other than the normal non-exclusive, royalty-free license to use the material. We reserve the right to take legal action for noncompliance with abovementioned requirements, unauthorized use, or other illegal or malicious use of the material.

Trademarks

Except as otherwise set forth herein, nothing in this document shall be construed as conferring any rights to use any trademark, trade name or name, abbreviation, or counterfeit product thereof owned by Quectel or any third party in advertising, publicity, or other aspects.

Third-Party Rights

This document may refer to hardware, software and/or documentation owned by one or more third parties (“third-party materials”). Use of such third-party materials shall be governed by all restrictions and obligations applicable thereto.

We make no warranty or representation, either express or implied, regarding the third-party materials, including but not limited to any implied or statutory, warranties of merchantability or fitness for a particular purpose, quiet enjoyment, system integration, information accuracy, and non-infringement of any third-party intellectual property rights with regard to the licensed technology or use thereof. Nothing herein constitutes a representation or warranty by us to either develop, enhance, modify, distribute, market, sell, offer for sale, or otherwise maintain production of any our products or any other hardware, software, device, tool, information, or product. We moreover disclaim any and all warranties arising from the course of dealing or usage of trade.

Disclaimer

- a) We acknowledge no liability for any injury or damage arising from the reliance upon the information.
- b) We shall bear no liability resulting from any inaccuracies or omissions, or from the use of the information contained herein.
- c) While we have made every effort to ensure that the functions and features under development are free from errors, it is possible that they could contain errors, inaccuracies, and omissions. Unless otherwise provided by valid agreement, we make no warranties of any kind, either implied or express, and exclude all liability for any loss or damage suffered in connection with the use of features and functions under development, to the maximum extent permitted by law, regardless of whether such loss or damage may have been foreseeable.
- d) We are not responsible for the accessibility, safety, accuracy, availability, legality, or completeness of information, advertising, commercial offers, products, services, and materials on third-party websites and third-party resources.

Copyright © Quectel Wireless Solutions Co., Ltd. 2021. All rights reserved.

About the Document

Revision History

Version	Date	Author	Description
-	2021-08-31	Anthony LIU	Creation of the document
1.0.0	2021-08-31	Anthony LIU	Preliminary

Contents

About the Document	3
Contents.....	4
1 Reference Design.....	5
1.1. Introduction	5
1.2. Schematics	5

1 Reference Design


1.1. Introduction

This document provides the reference design for Quectel EC200A series module. And the reference design includes block diagrams of power supply and module design, analog audio interfaces, (U)SIM interface, SD card interface design, etc.

1.2. Schematics

The schematics illustrated in the following pages are provided for your reference only.

Reference Design Block Diagram

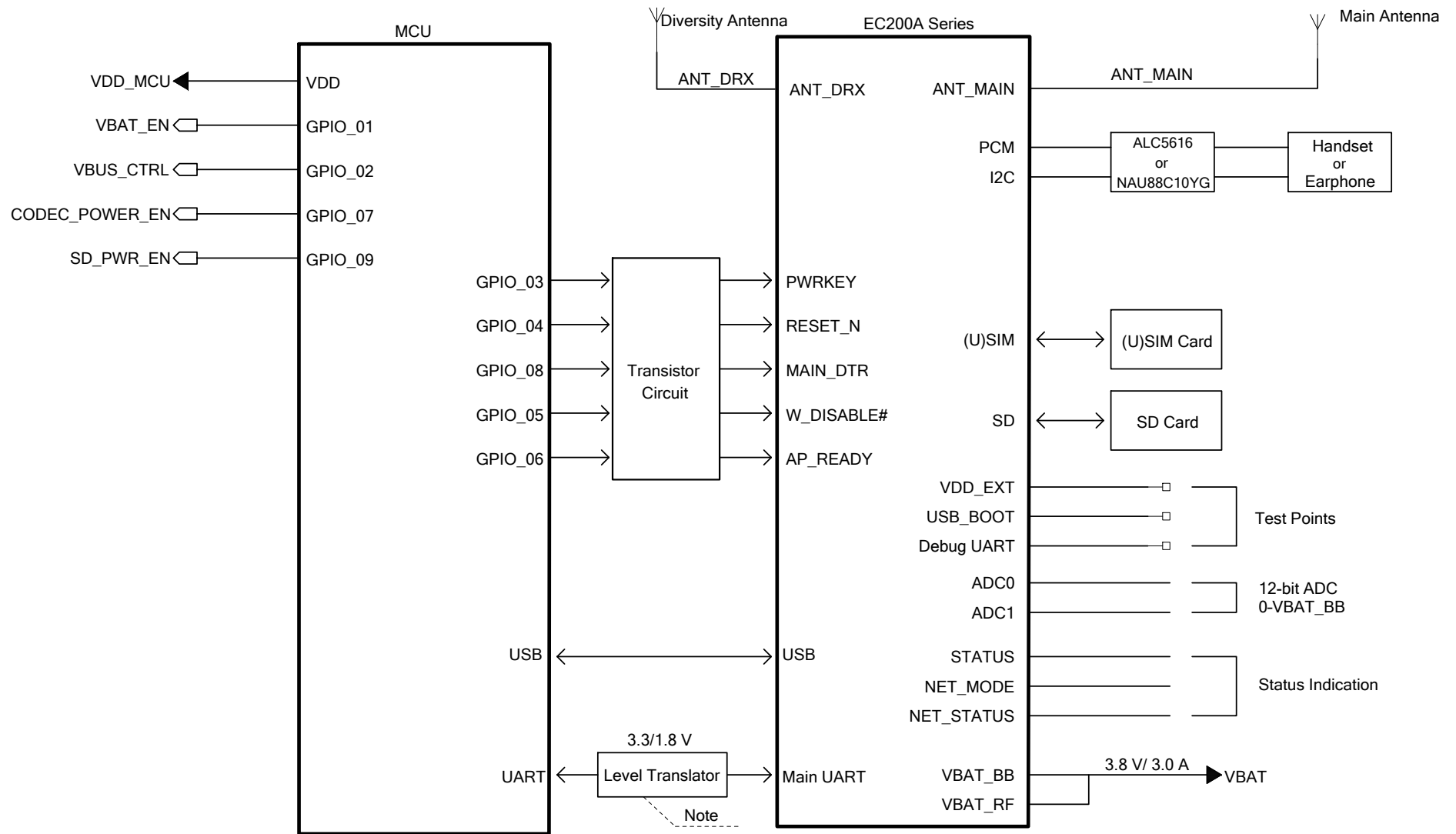


NOTE:

A level-shifting circuit with triode or a level translator TXS0108EPWR provided by Texas Instruments is recommended.


Quectel Wireless Solutions		
DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 1 OF 12	DATE 2021/8/31	

Power Supply Block Diagram

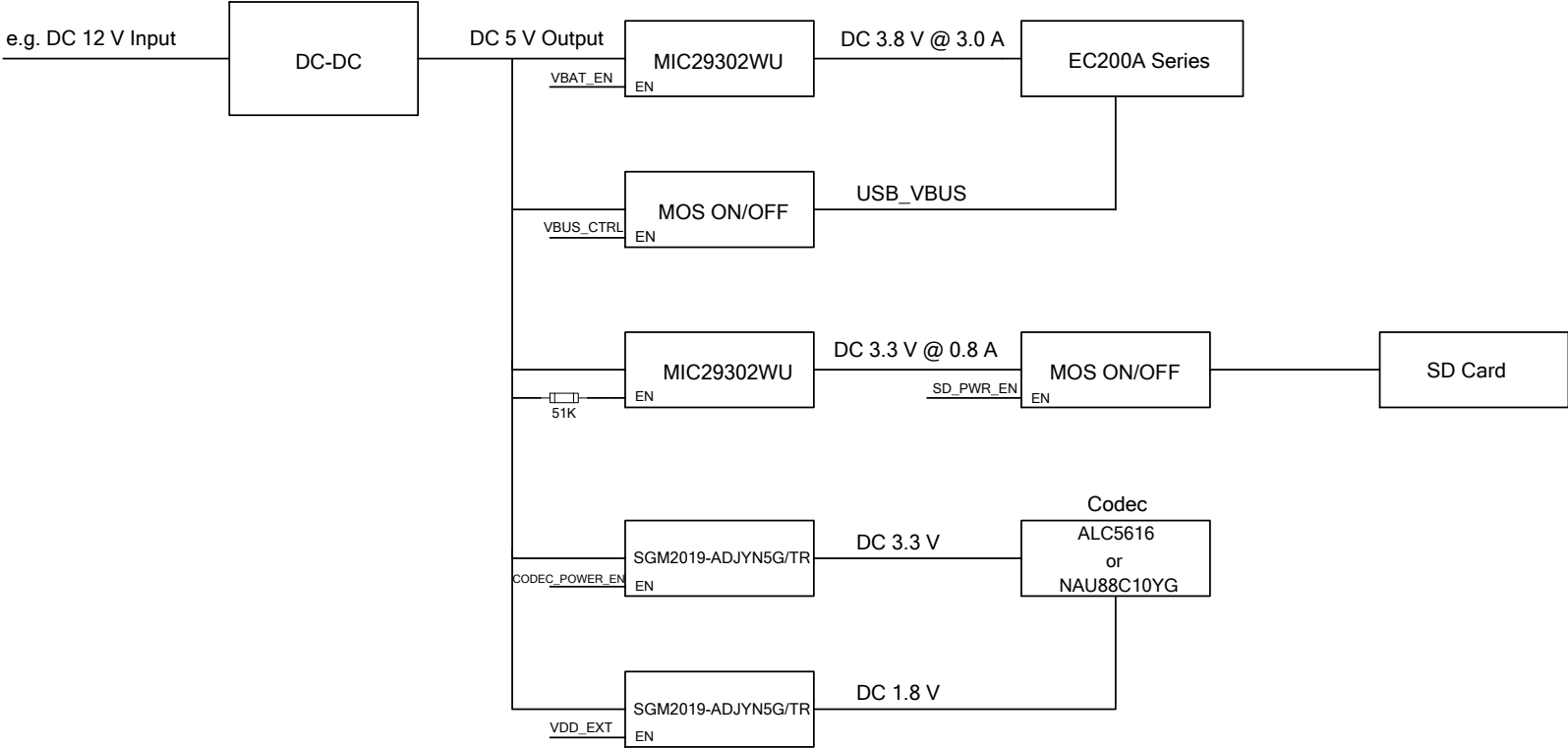

Quectel Wireless Solutions		
DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 2 OF 12		DATE 2021/8/31

Module Interface


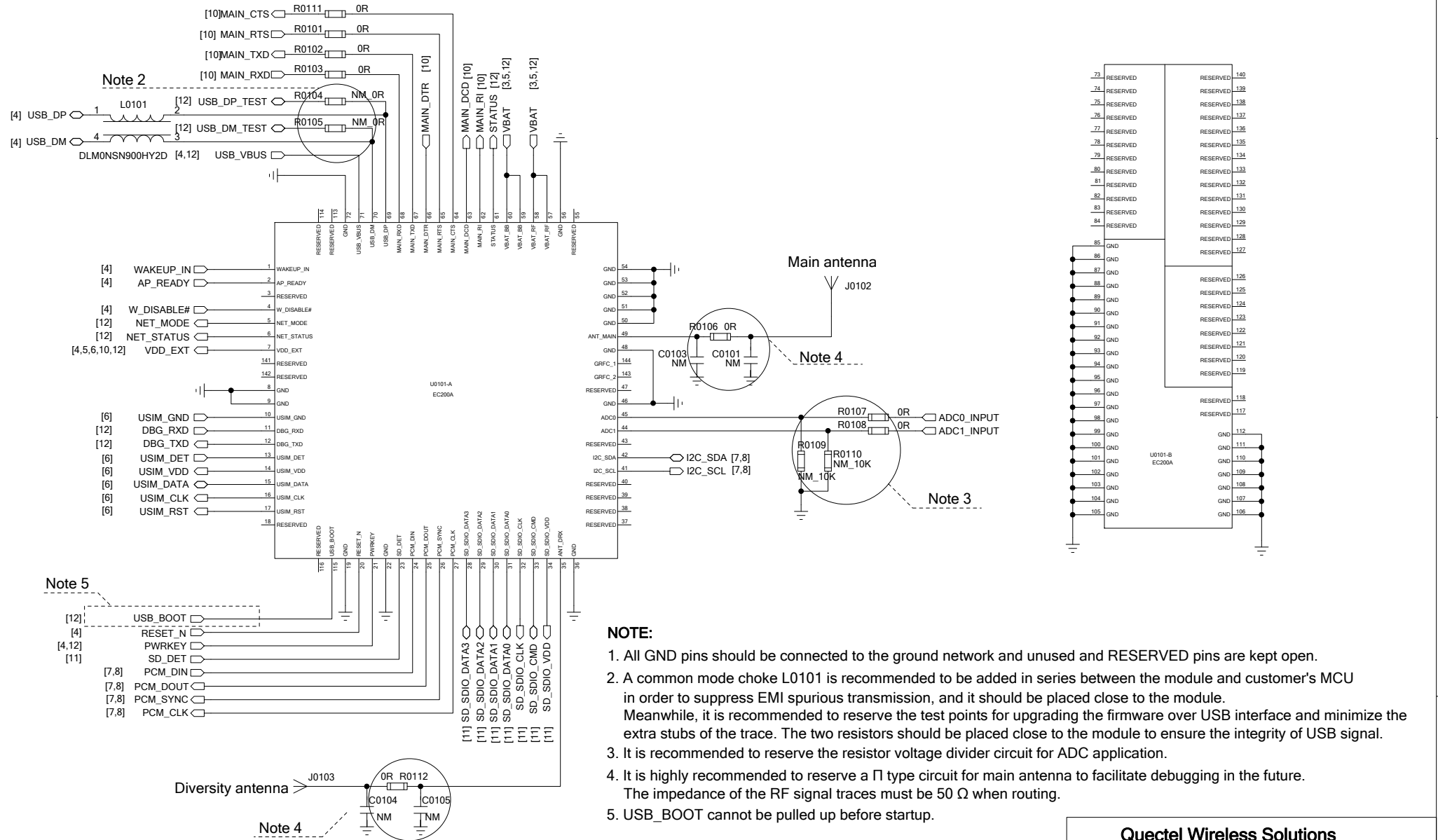


NOTE:

1. All GND pins should be connected to the ground network and unused and RESERVED pins are kept open.
2. A common mode choke L0101 is recommended to be added in series between the module and customer's MCU in order to suppress EMI spurious transmission, and it should be placed close to the module. Meanwhile, it is recommended to reserve the test points for upgrading the firmware over USB interface and minimize the extra stubs of the trace. The two resistors should be placed close to the module to ensure the integrity of USB signal.
3. It is recommended to reserve the resistor voltage divider circuit for ADC application.
4. It is highly recommended to reserve a Π type circuit for main antenna to facilitate debugging in the future. The impedance of the RF signal traces must be 50 Ω when routing.
5. USB_BOOT cannot be pulled up before startup.

Quectel Wireless Solutions		
DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY John SUN	SIZE A2	VER 1.0.0
SHEET 3 OF 12	DATE 2021/8/31	

MCU Interface

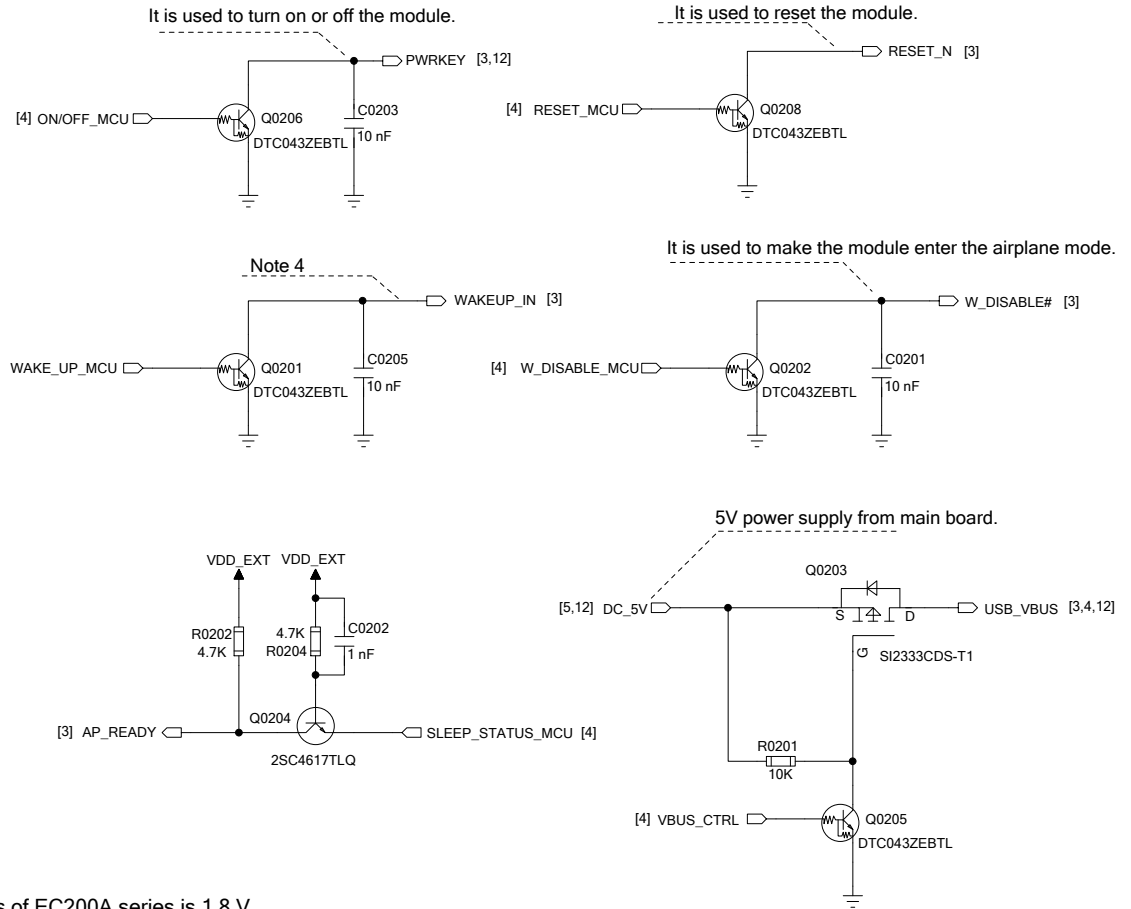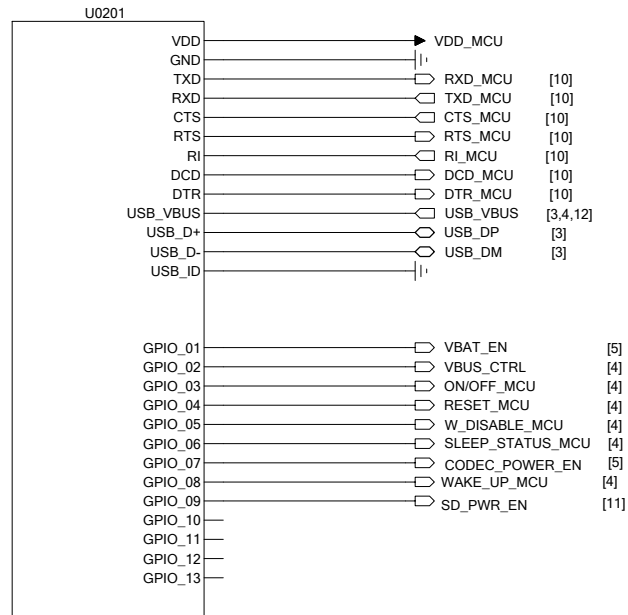

NOTE:


- U0201 represents customer's MCU. The power domain of GPIO interfaces of EC200A series is 1.8 V. If the GPIO interfaces of U0201 is also 1.8 V, then the related level-shifting circuit is not needed.
- The USB interface of EC200A series only serves as a slave device and supports full-speed and high-speed modes. To communicate with the USB interface, MCU needs to support USB host mode or OTG function. The USB_VBUS pin of the module should be powered by an external power system for USB detection, and VBUS_CTRL is used to turn on/off the USB_VBUS power supply.
- It is recommended to select GPIO pins which are at low level by default as the control pins for PWRKEY and RESET_N of the module. Ensure that the load capacitance does not exceed 10 nF on PWRKEY and RESET_N pins.

Quectel Wireless Solutions		
DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 4 OF 12	DATE 2021/8/31	


Power Supply Design

DC-DC Application

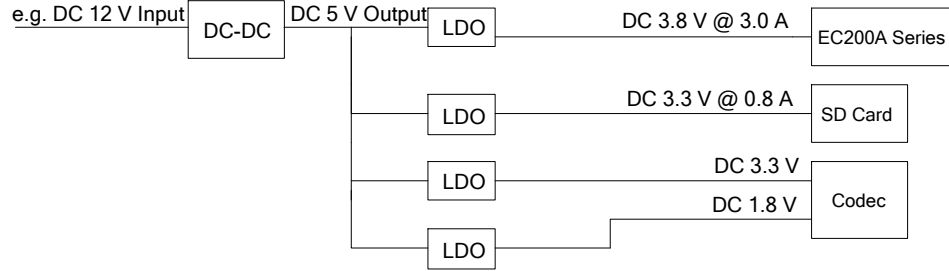When the input voltage is above 7.0 V, use a DC-DC converter to convert the input voltage into a 5.0 V output, and then use an LDO to convert it to 3.8 V, 3.3 V and 1.8 V.



VBAT Design

 


NOTE:

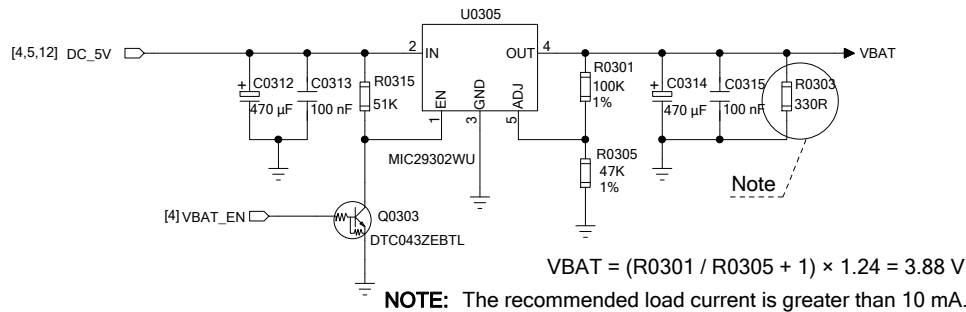
1. The VBAT supply current must meet the rated output capacity of 3.0 A. If you use a model that does not support the GSM frequency band, you can select a power supply with a current capability of 2.0 A.
2. VBAT should be routed in star configuration to VBAT_BB and VBAT_RF pins.
3. The recommended operating voltage of VBAT is 3.4-4.3 V.

LDO Application


When the input voltage is below 7.0 V, use an LDO to convert the input voltage to 3.8 V.



Power Supply for SD Card

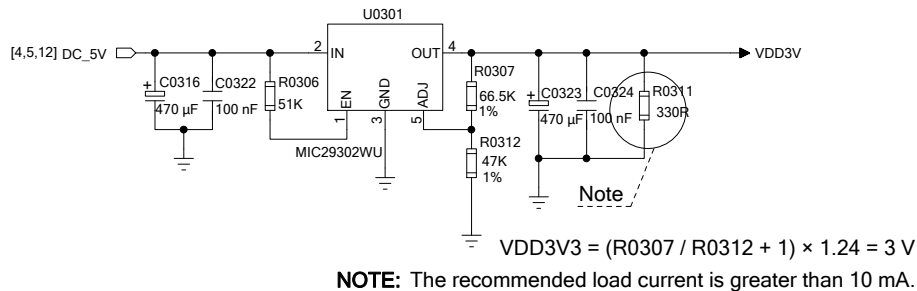

Power Supply for PCM Codec

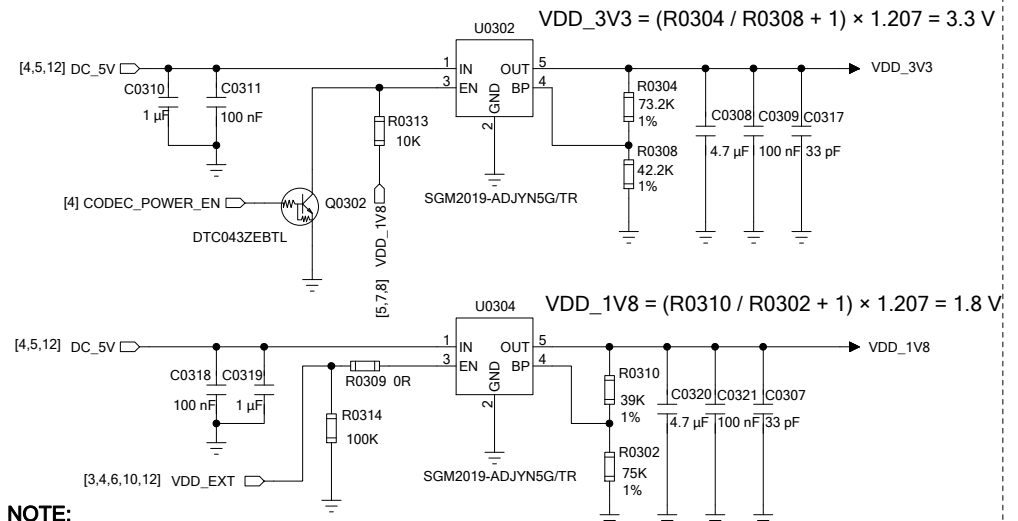


NOTE:

1. CODEC_POWER_EN must be at a low level in order to ensure the normal output voltage of VDD_3V3. If VDD_3V3 power supply needs to be switched off, please keep CODEC_POWER_EN at high level.
2. The following power-up/down sequences should be followed to ensure the audio codec works normally.
 Power-up Sequence: power up VDD_1V8 first, then VDD_3V3.
 Power-down Sequence: power down VDD_3V3 first, then VDD_1V8.

Quectel Wireless Solutions

DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY John SUN	SIZE A2	VER 1.0.0
SHEET 5 OF 12		DATE 2021/8/31

(U)SIM Interface Design

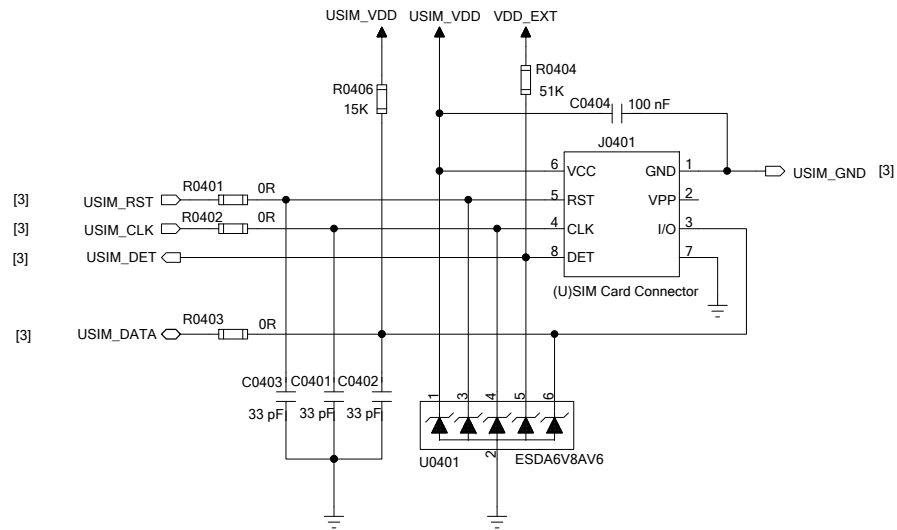


NOTE:

- U0401 is recommended to be used to offer good ESD protection, and the parasitic capacitance should be less than 15 pF.
- The GND of the (U)SIM card connector is recommended to be connected to the module's USIM_GND. In addition, USIM_GND can also be connected to the GND of customers' PCB directly if the PCB's GND is complete.
- The pull-up resistor R0406 of USIM_DATA can improve anti-jamming capability, and should be placed close to the (U)SIM card connector.
- Connect 0R resistors R0401-R0403 in series between the module and (U)SIM card for debugging; Capacitors C0401-C0403 can be used to filter out EGSM900 interference.
- C0404's capacitance should be less than 1 μ F and it should be placed close to the (U)SIM card connector.
- For more information about the layout of (U)SIM interface, please refer to *Quectel_EC200A_Series_Hardware_Design*.

Quectel Wireless Solutions

DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 6 OF 12		DATE 2021/8/31

Audio Codec Design (ALC5616)

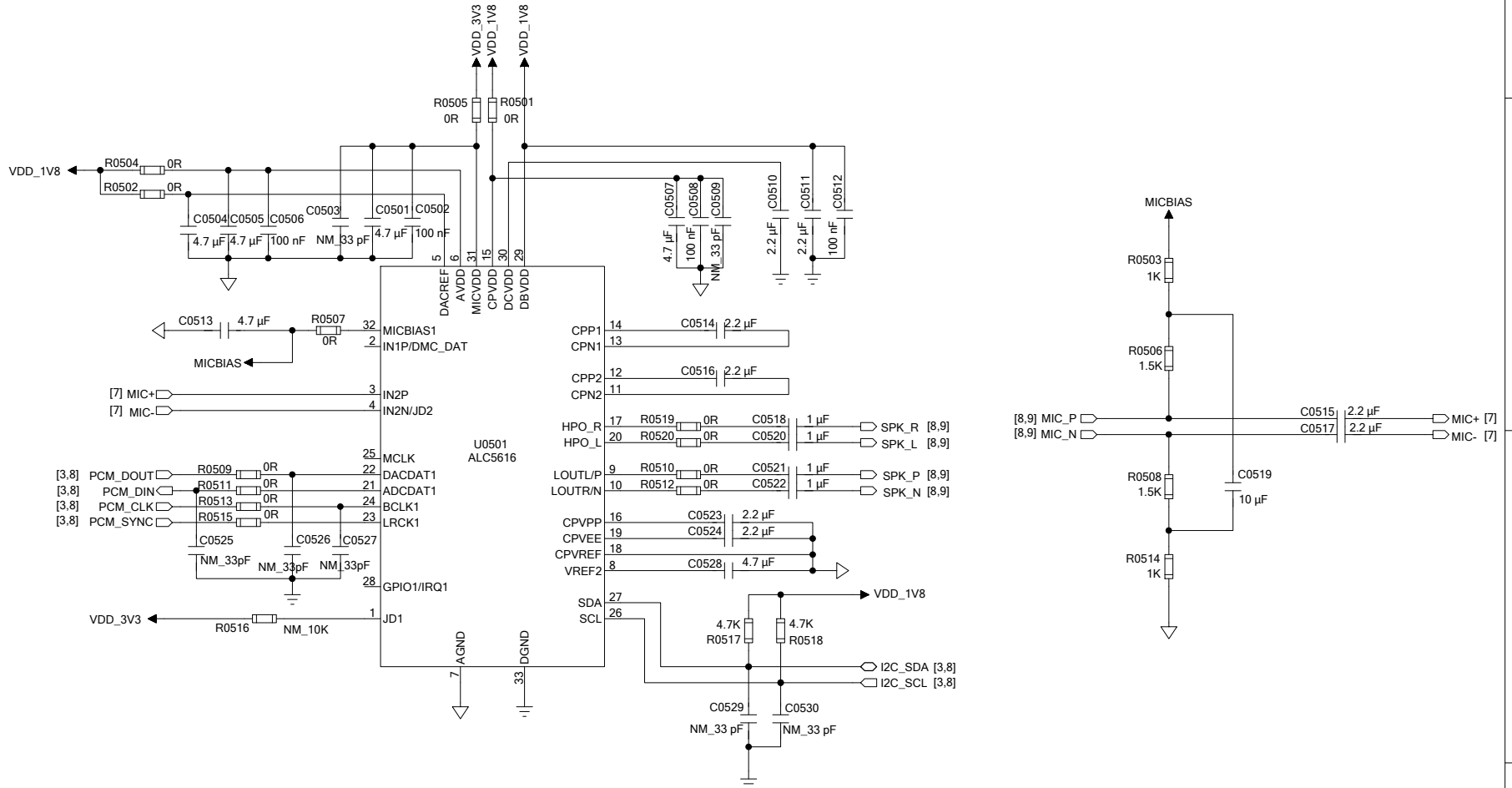


NOTE:

1. ALC5616 power-up sequence: DBVDD/I2C pull-up power/AVDD/DACREF/CPVDD → MICVDD → software initialization.
2. ALC5616 power-down sequence: disable codec function by software → MICVDD → DBVDD/I2C pull-up power/AVDD/DACREF/CPVDD.
3. The module will automatically initialize the codec via I2C interface after it is turned on successfully, so all power supplies for the codec need to be powered on before that.
4. The analog ground and digital ground need to be connected with a 0 Ω resistor R-0805. For more details, please refer to sheet "Audio Codec Design (Analog Interfaces)".

Quectel Wireless Solutions		
DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 7 OF 12	DATE 2021/8/31	

Audio Codec Design (NAU88C10YG)

Pin No.	Pin Name	Voltage	Description
2	VDDA	2.5-3.6 V	Analog VDD
4	VDDD	1.71-3.6 V	Digital VDD
17	VDDSPK	2.5-5.5 V	SPK power supply

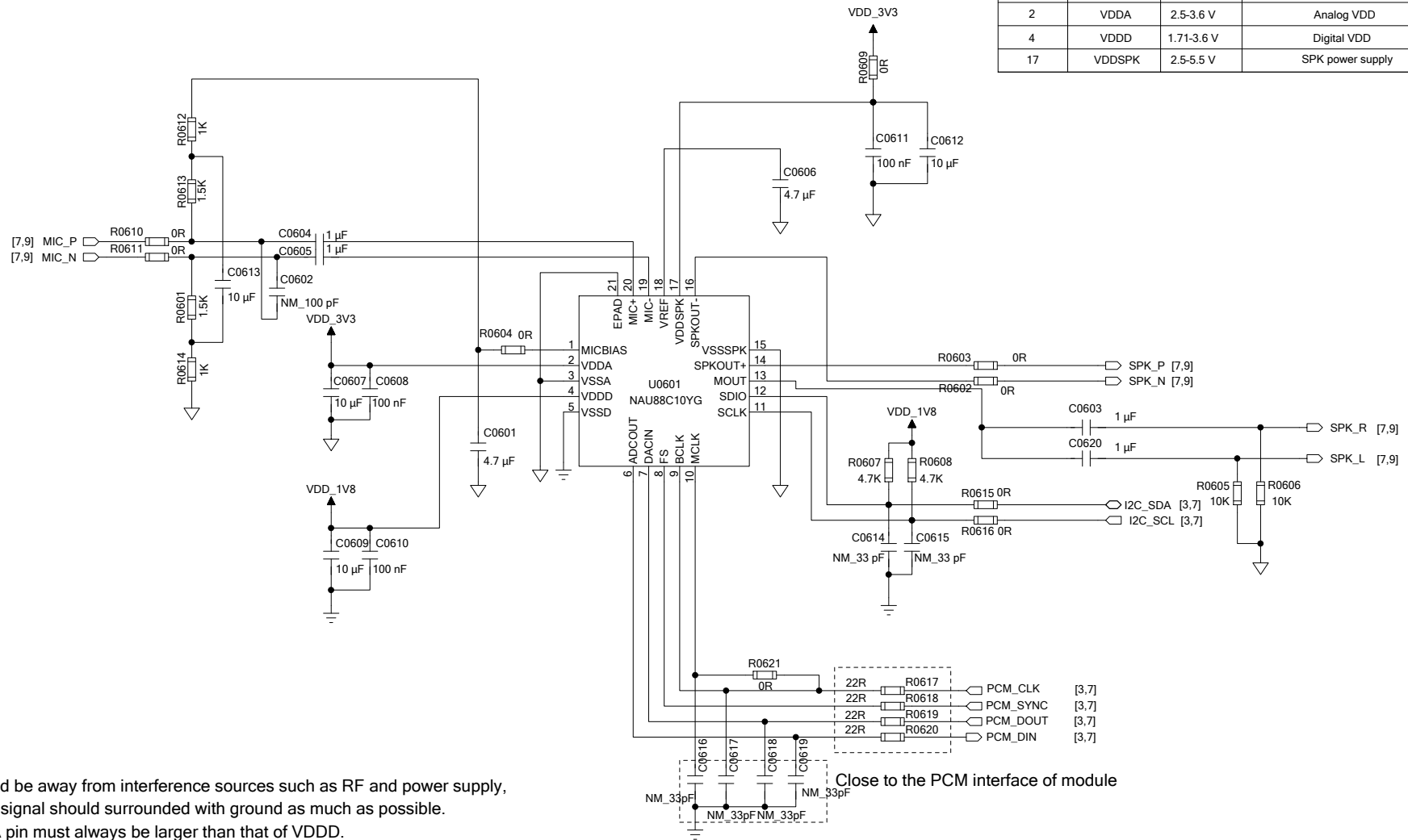


- NOTE:**
1. The codec part should be away from interference sources such as RF and power supply, and the codec audio signal should be surrounded with ground as much as possible.
 2. The voltage of VDDA pin must always be larger than that of VDDD.
 3. The analog ground and digital ground need to be connected with a 0 Ω resistor R-0805. For more details, please refer to sheet "Audio Codec Design (Analog Interfaces)".

Close to the PCM interface of module


Quectel Wireless Solutions		
DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 8 OF 12		DATE 2021/8/31

Audio Codec Design (Analog Interfaces)

Handset Application

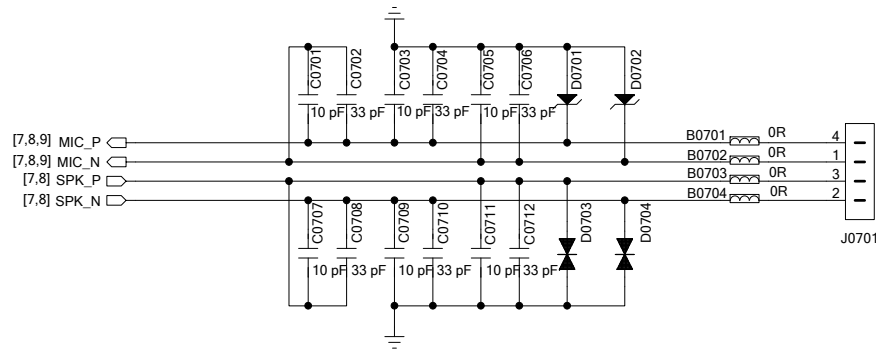

Earphone Application

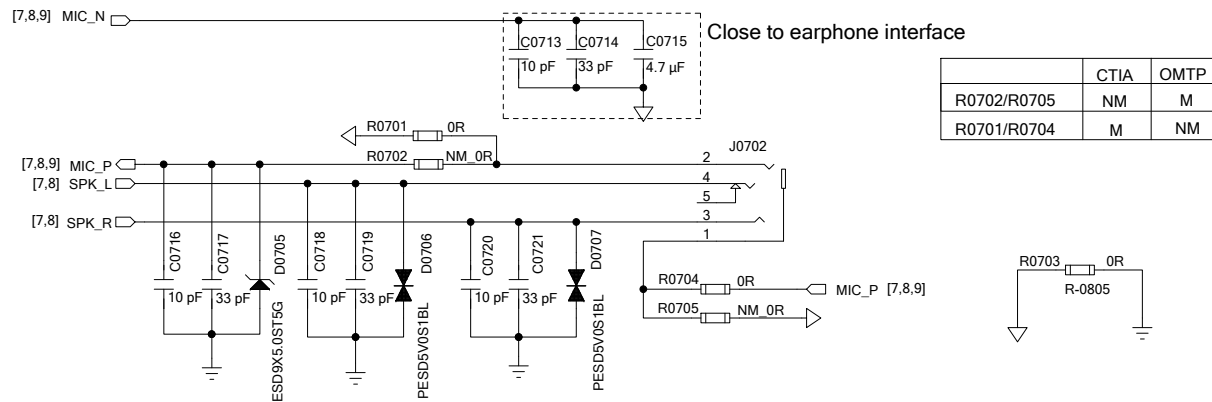

NOTE:


1. The analog output only drives handset and earphone. For larger power loads such as loudspeaker, an audio power amplifier should be added in the design.
2. In handset application, both the MIC and SPK signal traces need to be routed as differential pairs.
3. In earphone application, the MIC signal traces need to be routed as a differential pair.
4. All MIC and SPK signal traces should be surrounded with ground on the layer and ground planes above and below, and far away from noises such as clock and DC-DC signals, etc.
5. ALC5616 and NAU88C10YG, you can only choose one in audio codec design.

Quectel Wireless Solutions


DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET 9 OF 12		DATE 2021/8/31

UART Interfaces Design

UART Translation - Transistor Solution

 

UART Translation - IC Solution

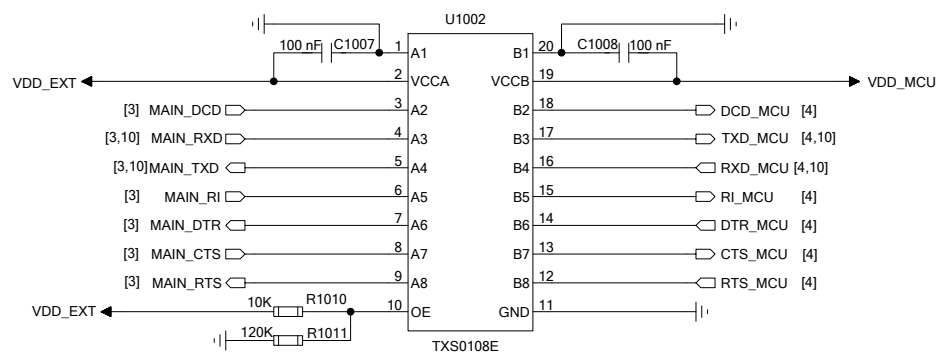


NOTE:

- There are two translation solutions: transistor solution and IC solution, and it is recommended to select the latter.
- The power supply of TXS0108E's VCCA should not exceed that of VCCB. For more information, please refer to the datasheet from TI.
- The transistor solution is not suitable for applications with baud rates exceeding 460 kbps. The capacitors C1002 and C1003 of 1 nF can improve the signal quality.
- MAIN_RTS and MAIN_DTR transistor circuits are similar to that of the MAIN_RXD interface. MAIN_CTS, MAIN_RI and MAIN_DCD transistor circuits are similar to that of the MAIN_TXD interface.

Quectel Wireless Solutions

DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET	10 OF 12	DATE 2021/8/31

SD Card Interface Design

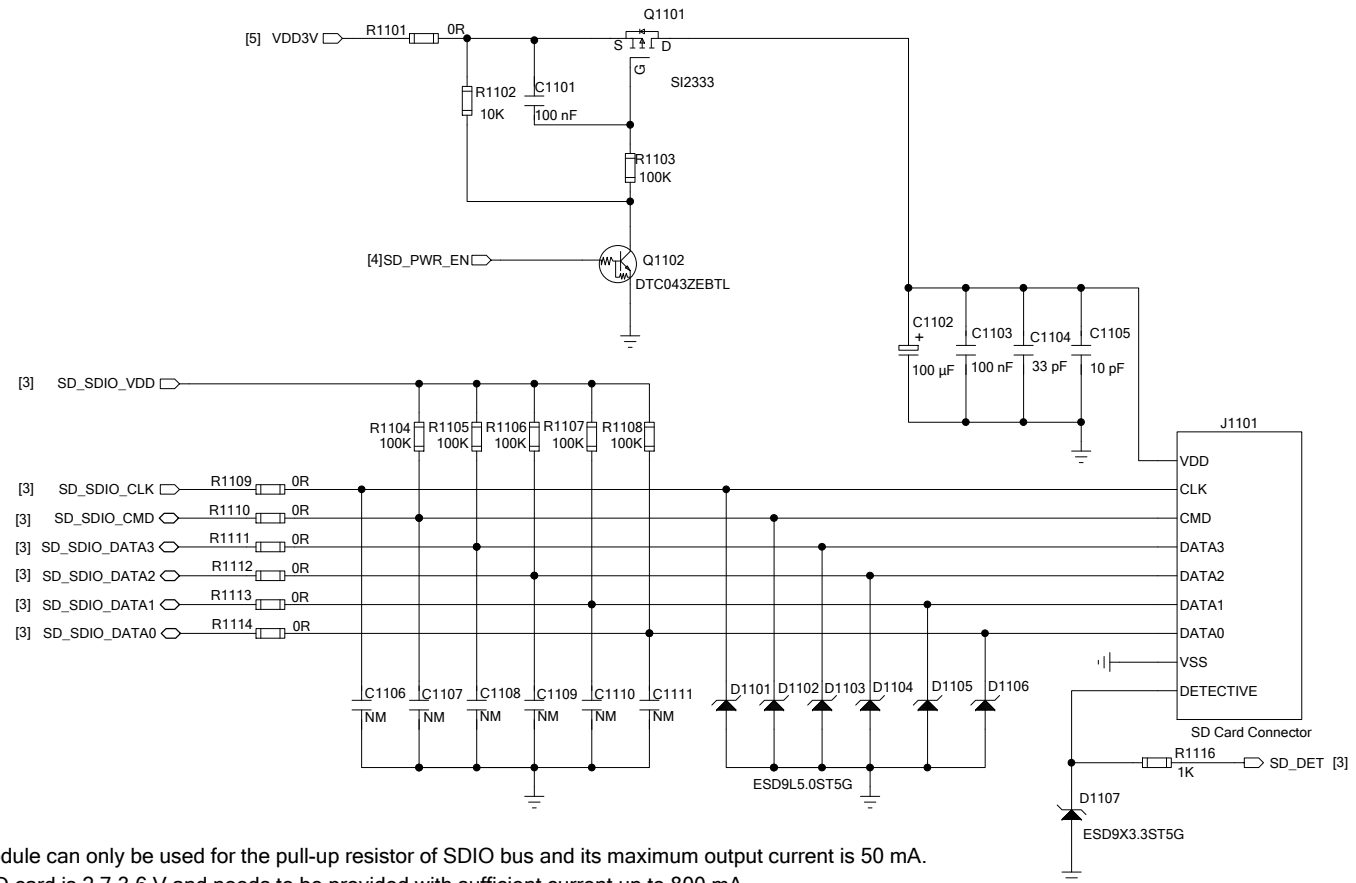

NOTE:


1. The pin 34 (SD_SDIO_VDD) on the module can only be used for the pull-up resistor of SDIO bus and its maximum output current is 50 mA.
2. The supply voltage range of VDD for SD card is 2.7-3.6 V and needs to be provided with sufficient current up to 800 mA.
3. To avoid the jitter of bus, pull-up resistors R1104-R1108 are recommended to be added to SDIO bus. SD_SDIO_VDD should be used as the pull-up power. The values of these resistors are among 10-100 kΩ and the recommended value is 100 kΩ.
4. In order to adjust the signal quality, it is recommended to add 0 Ω resistors R1109-R1114 in series between the module and the SD card connector. The bypass capacitors C1106-C1111 are reserved and not mounted by default.
5. It is recommended to add ESD protection components near the pins of SD card connector. The parasitic capacitance of ESD protection components should be smaller than 15 pF.
6. Keep SDIO signals far away from other sensitive circuits/signals such as RF circuits, analog signals, etc, as well as noisy signals such as clock and DC-DC signals, etc.
7. Route SDIO signals with 50 Ω ±10 % impedance. It is important to route SDIO signals surrounded with ground on the layer and ground planes above and below, and the total trace length should be less than 50 mm.
8. It is recommended to keep the trace length difference among SD_SDIO_CLK, SD_SDIO_DATA[0:3] and SD_SDIO_CMD less than 1 mm.
9. Make sure the adjacent trace spacing is two times the trace width and the bus capacitance is less than 15 pF.

Quectel Wireless Solutions

DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johen SUN	SIZE A2	VER 1.0.0
SHEET	11 OF 12	DATE 2021/8/31

Other Designs


Indicators

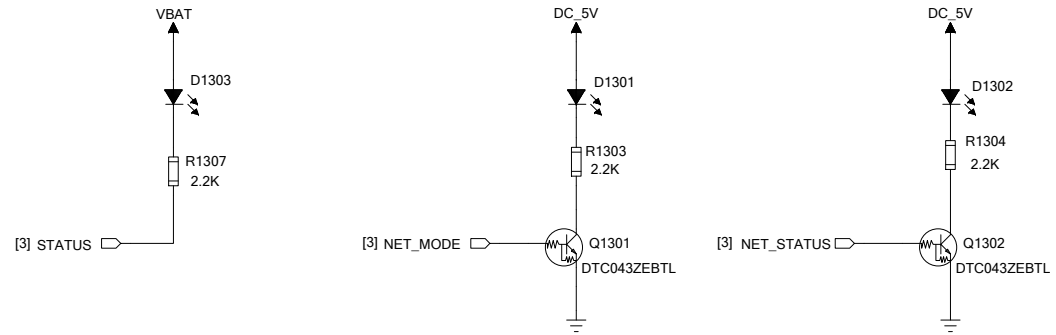

NOTE:

1. The STATUS is an open drain output pin.
2. For more details about NET_MODE and NET_STATUS, please refer to *Quectel_EC200A_Series_Hardware_Design*.
3. If the low current consumption is required when the customers' device is in sleep, replace the power supply VBAT and DC_5V of the STATUS, NET_MODE and NET_STATUS indicators with the external controllable ones, which can be turned off when the module is in sleep mode to reduce the power consumption.


Reserved Test Points

 

NOTE:

1. Test points for both USB and debug UART interfaces are reserved for catching logs.
2. Test points for USB interface also can be reserved for firmware upgrade.
3. The junction capacitance of the ESD protection components on USB data traces should be less than 2 pF.
4. The debug UART interface supports 1.8 V power domain, and a voltage-level translator should be used if the power domain of customers' application is 3.3 V.

Emergency Download

 

NOTE:

1. It is recommended to reserve the USB_BOOT interface design.
 2. USB_BOOT is kept open by default.
- Pull up USB_BOOT before VDD_EXT is powered on to make the module enter the emergency download mode after booting.

Quectel Wireless Solutions

DRAWN BY Anthony LIU	PROJECT EC200A Series	TITLE Reference Design
CHECKED BY Johnen SUN	SIZE A2	VER 1.0.0
SHEET	12 OF 12	DATE 2021/8/31